



M – 2019

Subject Code : 40 (NS)

2101690

ELECTRONICS

Time : 3 Hours 15 Minutes]

[Total No. of questions : 37]

[Max. Marks : 70

- Instructions :**
- i) Question paper has four Parts A, B, C and D.
 - ii) Part - A has no choice.
 - iii) Part - D has two Parts.
Part - I is from problems
Part - II is of essay type questions.
 - iv) Circuit diagram/timing diagram/truth tables are drawn wherever necessary.
 - v) Problems without necessary formula carry no mark.

PART – A

Answer **all** questions :

(10 × 1 = 10)

- 1) Name the charge carriers in N-channel JFET.
- 2) Write the value of bandwidth of an ideal OPAMP.
- 3) Draw the waveform of damped oscillations.
- 4) What is the function of transmitter in a radio communication system?

P.T.O.

40 (NS)

-2-



- 5) Draw the waveform of AM wave when modulation index $m_a = 1$.
- 6) Define fidelity in a radio receiver.
- 7) Mention one application of TRIAC.
- 8) Write the decimal equivalent of BCD code $(00110101)_2$.
- 9) Name any one arithmetic operator in C-language.
- 10) Expand RADAR.

PART – B

Answer **any five** questions :

(5 × 2 = 10)

- 11) Mention the steps to obtain DC-equivalent circuit of a CE amplifier.
- 12) Calculate the gain of a negative feedback amplifier with an internal gain, $A = 100$ and feedback factor $\beta = 1/10$
- 13) Write any two applications of crystal oscillator.
- 14) Realise XOR gate using basic logic gates.
- 15) Write the difference between combinational and sequential logic circuits.



- 16) Write any two instruction set of 8051 microcontroller.
- 17) Mention any two features of C-language.
- 18) Briefly explain the internet.

PART – C

Answer **any five** questions :

(5 × 3 = 15)

- 19) Compare the FET and BJT.
- 20) What is a transistor biasing? Briefly explain the need for biasing a transistor.
- 21) With a block diagram derive an expression for output impedance of a amplifier with negative feedback.
- 22) Explain the importance of ionosphere in the radio communication.
- 23) Derive an expression for the total power of AM wave.
- 24) In a SCR full wave rectifier the firing angle is 90° , rms voltage of an input to the rectifier is 230 V and the load resistance is 25Ω . Calculate V_{dc} and I_{dc} .

40 (NS)

-4-



25) With a neat circuit diagram explain the working of power diode under forward bias condition.

28) C


26) With a neat block diagram explain the satellite Transponder.

PART - D

I. Answer any three questions :


(3 × 5 = 15)

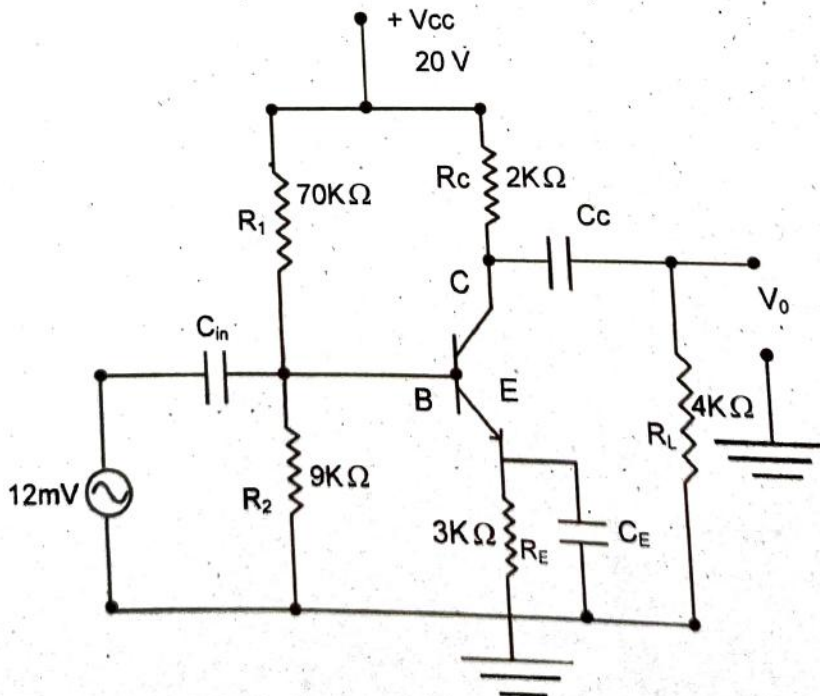27) Calculate voltage gain (A_V) and input impedance (Z_{in}) of a given CE amplifier with values $r_e' = \frac{26 \text{ mV}}{I_E}$, $V_{BE} = 0.7 \text{ V}$, $\beta = 100$





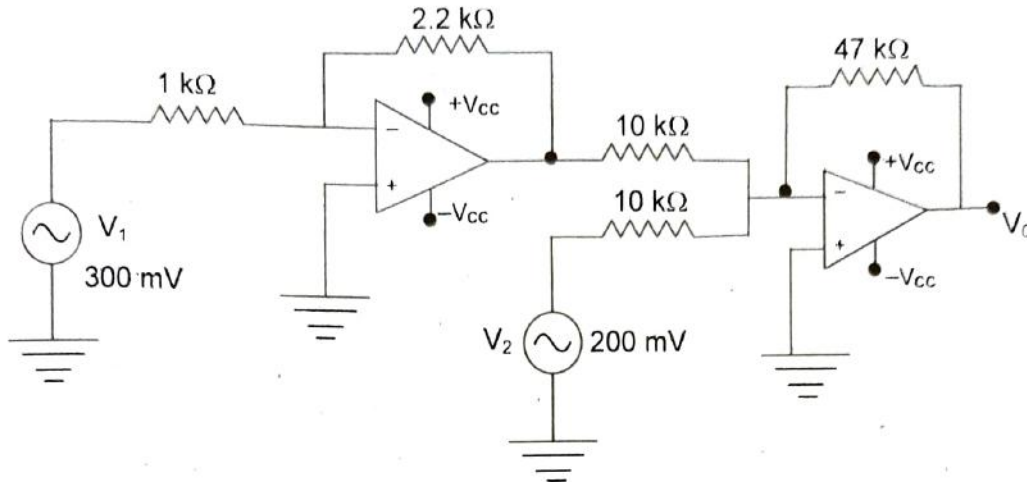28) Calculate the output voltage (V_0) for a given circuit below.



29) A transistor Colpitts oscillator has $L = 4 \text{ mH}$, $C_1 = 10 \text{ nF}$ and $C_2 = 10 \text{ nF}$. Calculate the frequency of oscillations.

30) The current of a AM transmitter is 8A when the carrier is sent, it increases to 8.65 A when the carrier is modulated. Find the percentage of modulation. Also calculate the antenna current when the depth of modulation is 0.75.

31) Simplify the Boolean expression using K-map.

$$Y(ABCD) = \sum m(0, 2, 4, 5, 8, 10, 12, 14) + \sum d(6, 13)$$

Write the logic circuit for the simplified expression.



II. Answer **any four** questions:

32) Compare CE, CB and CC amplifiers.

33) a) What are active filters?

(1 + 4)

b) With a neat circuit diagram explain the working of first order low pass active filter and draw its frequency response curve.

34) Draw a block diagram and explain the different stages of FM transmitter.

35) a) What is flip-flop?

b) With a logic diagram and truth table, explain the working of SR flip-flop..

(1 + 4)

36) Write a flow chart and explain the steps used in creating assembly language program in 8051 microcontroller.

37) Write a C-program to find largest among three numbers.
